

## Homework 4

**Due Date: April 20**


There is nothing to hand in for this homework assignment. There will be a short quiz at the **beginning of class** on the indicated date. The solution sheet will be posted on the course web page.

Do text problems (you may want to do the additional problems below **first**):

4.1, 4.5\*, 4.7.1\*-4.7.3\*, 4.7.6\*, 4.16.1-4.16.3

\* Refer to Figure 4.17, which is a single-cycle data path. Also note that Figure 4.12 may have an error (depending on when your book was printed): The column labeled **ALU control input** should read **ALU control output**.

In addition:

 

Suppose a three-bit control signal determines the output of a two-input multiplexor, as shown above. If we call the three bits A, B, and C, assume line 1 (true) of the multiplexor is chosen if

$((A \text{ OR } B) \text{ OR } C) \text{ OR } (A \text{ AND } C) \text{ OR } (A \text{ AND } B)$ .

1. [5] Implement the logic for the control signal. Your circuit should directly implement the given expression (do not “optimize” it) using two-input AND and OR gates.
2. [5] Suppose the latency of an AND gate is 28ps (ps = picosecond) and the latency of an OR gate is 35ps. What is the length of the critical path of your circuit?